

I pledge on my honor that I have not given or received any unauthorized assistance on this test.

Name & date _____

1. In a series circuit, the total resistance is calculated by ____.

- a. adding the reciprocal of each resistor's value
- b. adding the values of all resistors
- c. multiplying the resistor values.
- d. dividing the voltage by the current

2. Kirchhoff's Voltage Law (KVL) states that the ____.

- a. total current in a circuit is constant.
- b. power generated is less than power dissipated
- c. sum of voltage rises equals the sum of voltage drops
- d. resistance is inversely proportional to voltage

3. When measuring voltage from point A to point B (V_{AB}), the ____ lead of the voltmeter is placed on point A.

- a. black
- b. red
- c. either lead
- d. ground

4. In a series circuit with multiple voltage sources, you determine the net voltage by ____.

- a. multiplying the voltages
- b. adding the voltages if they are in the same direction
- c. subtracting the voltages if they are in opposite directions
- d. b and c

5. If a voltage source has current flowing into its positive terminal, it is ____.

- a. acting as a resistor
- b. being charged
- c. short-circuiting
- d. is generating maximum power

6. The current in a series circuit ____.

- a. splits between the resistors
- b. changes depending on the resistance
- c. is the same through all resistors
- d. is zero.

7. If the voltage across a 250- Ω resistor is 2.5 V and the voltage across a 750- Ω resistor is 7.5 V in a series circuit, the total voltage applied is ____.

- a. 10
- b. 7.5
- c. 2.5
- d. 12.5

8. If the current flowing through a 1k Ω resistor is 10 mA, the voltage drop across the resistor is ____ V.

- a. 0.1
- b. 10
- c. 100
- d. 1,000

9. In a series circuit, the total power generated by the voltage source must be equal to the ____.

- a. sum of the currents
- b. sum of the voltages
- c. sum of the resistances.
- d. total power dissipated by the resistors

10. Reversing the polarity of one voltage source in a series circuit with two voltage sources, the ____.

- a. total current doubles
- b. total resistance increases
- c. net voltage becomes zero if the sources are equal
- d. total power increases